

**Analog IC Design Lab
COURSE PROJECT**

**Design and analysis of a 2-stage op-amp with
high gain bandwidth product**



Submitted by,
BODEPU KASI VISWANADHAM NAIDU
ROLL No - 234102411

EEE - VLSI & NANOELECTRONICS

Contents

1	EXPERIMENT	2
2	OBJECTIVE	2
2.1	General Design Specifications	2
2.2	High Gain Bandwidth Design Specifications	2
3	2 STAGE OPAMP	3
4	2 stage OPAMP design	4
4.1	Design procedure	4
5	RESULTS AND CONCLUSIONS	8
5.1	DC ANALYSIS	8
5.2	AC ANALYSIS	10
5.3	TRANSIENT ANALYSIS	13
6	CONCLUSIONS	17

1 EXPERIMENT

Design a 2-stage Op-amp in 180 nm technology targeting different applications.

2 OBJECTIVE

Design and analyze a 2-stage op-amp with a high GainBandwidth with the Design specification mentioned below.

2.1 General Design Specifications

- A Reference current source = $20\mu\text{A}$.
- Supply voltage = 1.8V .
- Slew Rate $\geq 1\text{ V}/\mu\text{s}$
- ICMR = $0.6\text{-}1.4\text{ V}$
- Load Capacitance $C_L = 10\text{ pF}$
- Phase Margin $\geq 60\text{ degrees}$

2.2 High Gain Bandwidth Design Specifications

- Gain $\geq 40\text{dB}$
- GBW $\geq 70\text{MHz}$
- Power Dissipation $\leq 1\text{mW}$
- $L \leq 2\mu\text{m}$

3 2 STAGE OPAMP

The operational amplifier as the name suggests is an amplifier with a certain operation. Here a 2 stage opamp implies two kinds of amplifiers are cascaded such as to achieve the characteristics of both the amplifiers.

In this experiment, a differential amplifier is cascaded with a common source amplifier to achieve a high gain, and for high gain bandwidth product. A two-stage operational amplifier consists of a differential amplifier at the input stage, while the second stage is a high gain stage biased by the output of the differential amplifier. As explained before, a two-stage operational amplifier exhibits two poles below the unity open-loop gain. There is a sta-

 


Figure 1: Circuit of 2 stage opamp

bility problem even though the two stages are compensated, when cascading the two stages, the circuit ends up with three high-impedance nodes. Consequently, two poles will be below the unit gain cross-over frequency, which will cause instability. Hence, introducing a single capacitor will dominate the other poles. So that the gain cross-over frequency will only be affected by one pole. The Poles and capacitance are known to be inversely proportional to each other. Therefore, a high capacitance must be introduced to create the dominating pole. To put it simply, we apply the Miller Theorem to one

capacitance. Therefore, it will offer a big capacitance with a little value, as C_c in the circuit above.

An amplifier's Gain Band Width Product is just the product of its Open Loop gain times the frequency range where its gain is reduced to -20 dB.

To calculate the suitable W/L ratio of each transistor in the above figure, the following process steps are used.

- Initially assuming a 60-degree phase margin and unity gain frequency is at least 10 times that of the provided gain bandwidth product. This assumption provides us with a miller capacitance of C_c at least $0.22C_L$.
- With the given slew rate which is the current through I5 over C_c , the current through MOSFET M5 is obtained.
- Using the gain bandwidth product, the gm for mosfet M1 is obtained which in turn provides us with the W/L ratio of M1 and M2 because both are symmetric.
- For the W/L ratio of M3 and M4, make use of the max ICMR as the gate voltage and use min ICMR to find the W/L ratio of M5.
- For M6, the gain bandwidth product is used such that the unity gain frequency is 10 times it. And since M6 and M4 are current mirrors the ratio of their aspect ratio is the same as the ratio of currents through them.
- similarly, M5 and M7 forms a current mirror.

4 2 stage OPAMP design

4.1 Design procedure

Step 1

Assuming that for a stable system, the phase margin is 60 degrees and zero frequency at greater than 5 times Gain Bandwidth product. So, by solving

the equation of one zero and two pole system, with the above Assumptions we got the equation,

$$C_c \geq 0.22C_L \quad (1)$$

They given C_L is 10 pF.so we got miller capacitance is

$$C_c > 2.2pF \quad (2)$$

Step 2

This design focuses on the high gain bandwidth of a two-stage opamp. One of the provided design parameters specified that the power *leq* 1mW and reference current source is 20μA.

$$\begin{aligned} power &\leq 1 * 10^{-3}W \\ 1.8 * (I_{ref} + I_5 + I_7) &\leq 10^{-3} \\ I_5 + I_7 &\leq 535.55\mu A \end{aligned}$$

Fixing I_5 is 80μA and I_7 is 440μA.

Step 3

$$slew - rate = \frac{I_5}{C_c} \quad (3)$$

Given slew rate minimum 1V/μs. Assumed the slew rate to be 20V/μs.

$$C_c = 4pF \quad (4)$$

Step 4

The gain bandwidth product is the voltage unit gain frequency. Because there is a dominant pole, there will be a 20dB decay at unit gain frequency.

$$gm_1 = 2\pi * GBW * C_c \quad (5)$$

then gm_1 is

$$gm_1 = 1759.291\mu A \quad (6)$$

with

$$gm_1 = \sqrt{2I_d\mu_n C_{ox} \frac{W}{L_1}} \quad (7)$$

substituting the values in the above equation then

$$\frac{W}{L_1} = 113.066 = \frac{W}{L_2} \quad (8)$$

Step 5

maximum ICMR is 1.4V. In the above circuit, for M1 to be in saturation

$$V_{d1} > V_g - V_{th1} \quad (9)$$

$$V_g < (V_{dd} - (V_{tp} + \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L} 3}}) + V_{th1} \quad (10)$$

here gate voltage is the maximum ICMR voltage. Substituting all the values

$$ICMR_{max} > (V_{dd} - (V_{tp} + \sqrt{\frac{2I_D}{\mu_p C_{ox} \frac{W}{L} 3}}) + V_{th1} \quad (11)$$

$$\frac{W}{L}_3 = \frac{W}{L}_4 > 3.6448 \quad (12)$$

Step 6

ICMR minimum is 0.4V. For all transistors to be in saturation.

$$V_{dsat} = ICMR_{min} - \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L} 1}} - V_{thn} \quad (13)$$

substituting all the values,

$$V_{dsat} = 0.0045V \quad (14)$$

But the minimum overdrive voltage should be 0.1V, V_{dsat} is assumed as 0.1V, then substituting the value in the current equation

$$\frac{W}{L}_5 = 46.76 \quad (15)$$

Step 7

M6 and M4 are in the current mirror.

$$\frac{(W/L)_6}{(W/L)_4} = \frac{I_6}{I_4} \quad (16)$$

this gives

$$\frac{W}{L}_6 = 40.095 \quad (17)$$

Step 8

$$\frac{(W/L)_7}{(W/L)_5} = \frac{I_7}{I_5} \quad (18)$$

M6 and M7 are in series so both currents are equal.

$$(W/L)_7 = 257.175 \quad (19)$$

and since both M5 and M8 form a current mirror with a ratio of currents 4:1.

$$(W/L)_8 = 11.69 \quad (20)$$

Now that all the (W/L) ratios have been found, individual transistor lengths are to be calculated. Since the optimization to be done on obtaining high bandwidth implies that the circuit is a high-frequency circuit. For high-frequency circuits, the design is done on minimum lengths so the length of transistors is considered as 360nm. Gain of two two-stage opamp is

$$gain = gm_1 gm_2 (r_{o1} || r_{o4}) (r_{o6} || r_{o7}) \quad (21)$$

5 RESULTS AND CONCLUSIONS

5.1 DC ANALYSIS

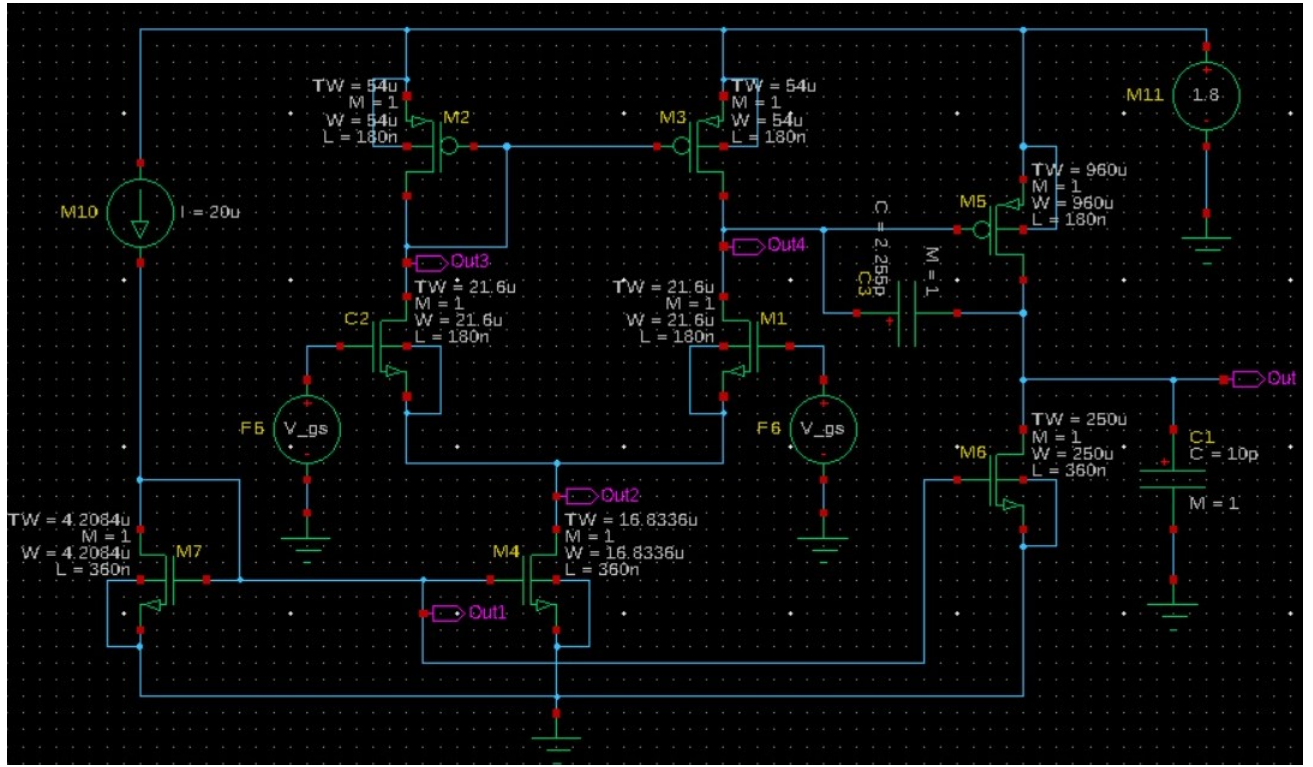


Figure 2: schematic of DC analysis

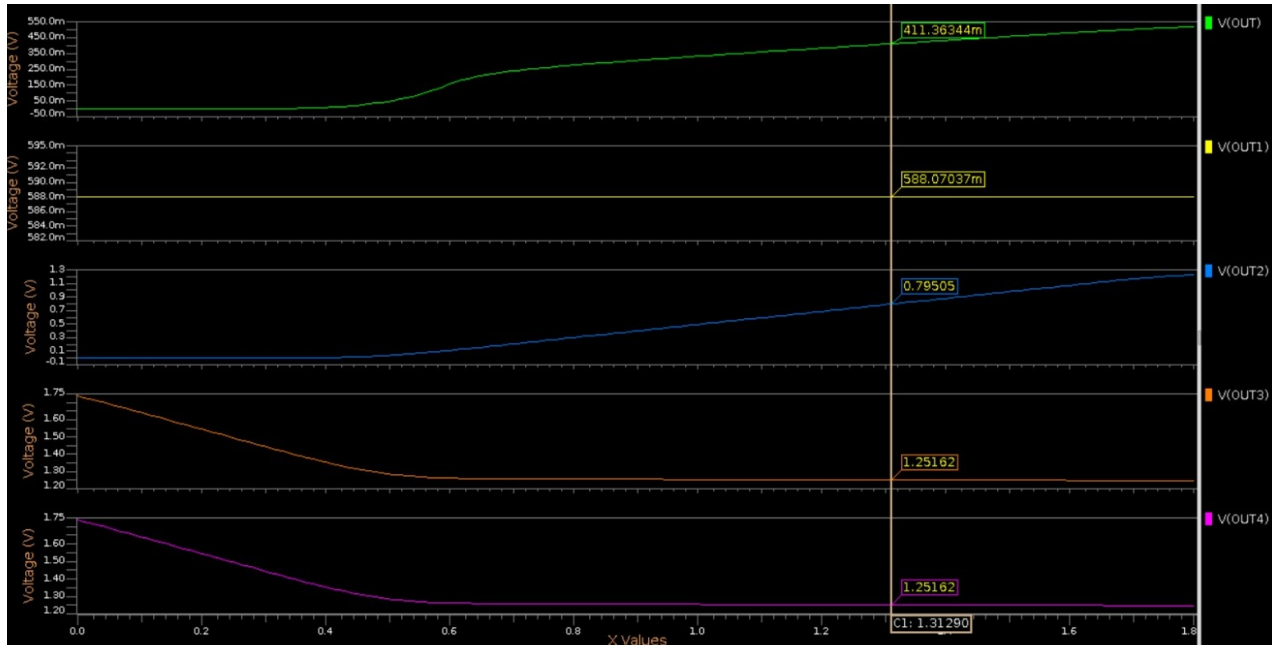


Figure 3: Operating Point for transistors in saturation

 


Figure 4: Operating Point for transistors in saturation

5.2 AC ANALYSIS

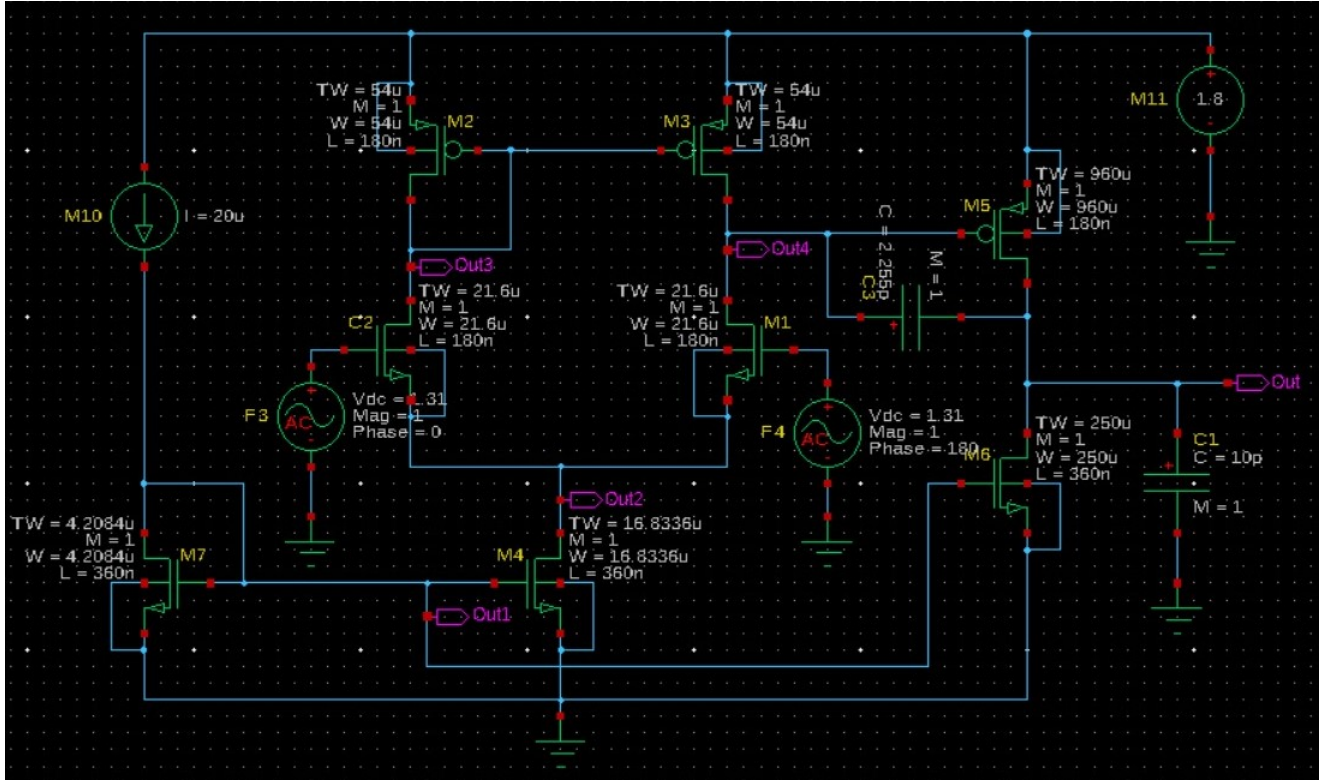


Figure 5: schematic of AC analysis

- To find the common mode gain, the same input is applied at both ends of the input. Then AC analysis is done to find the gain.
- To find PSRR the AC input is applied in place of Vdd, dc bias is applied at the input gate of the transistors and one branch input is connected to the output. AC analysis is then done and gain is found out.

 


Figure 6: Gain, Bandwidth, Unity gain frequency and phase margin

 


Figure 7: Common Mode Gain

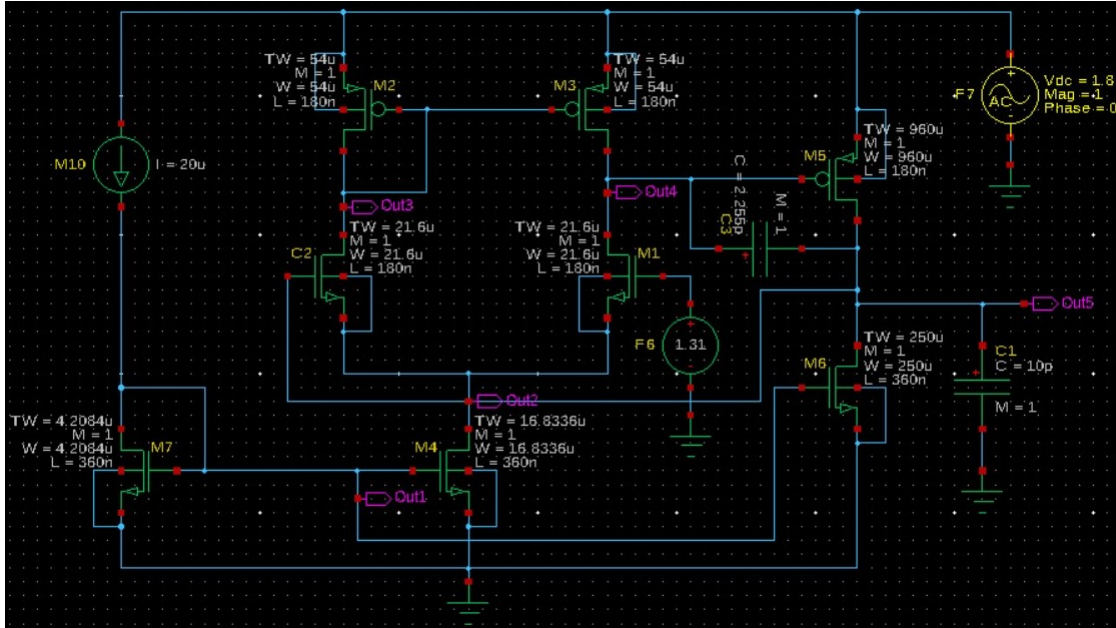


Figure 8: schematic of PSRR in AC analysis

 


Figure 9: Plot to measure PSRR

5.3 TRANSIENT ANALYSIS

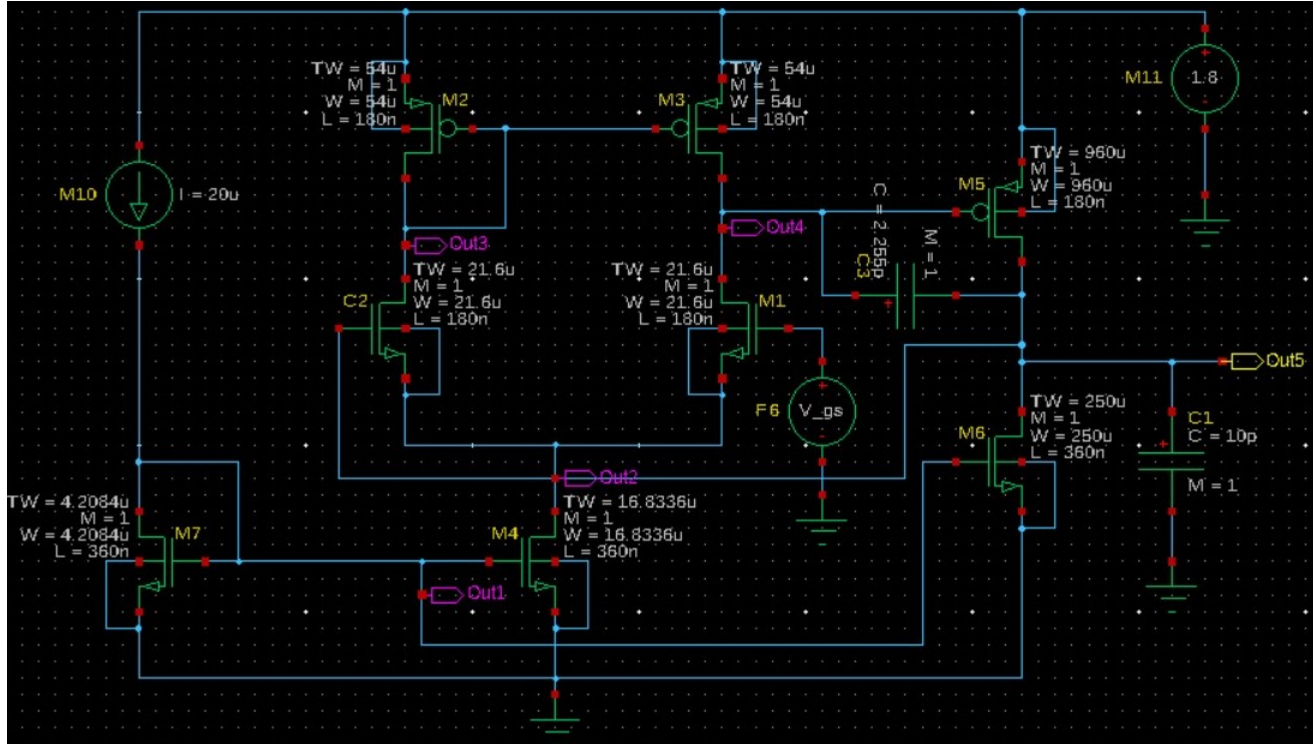


Figure 10: schematic of ICMR/OCMR analysis

- For ICMR and OCMR, The branch in which the output is sensed will be connected to the output, and a DC sweep is done to find the minimum to maximum input and minimum to maximum output.
- For Slew Rate, for a maximum slew rate the entire current should flow through only a single branch.; For that, a square pulse is input at one end and the other is grounded. Transient analysis is done then the max difference in output in a period gives the slew rate of the design implemented]

 


Figure 11: Plot for ICMR and OCMR

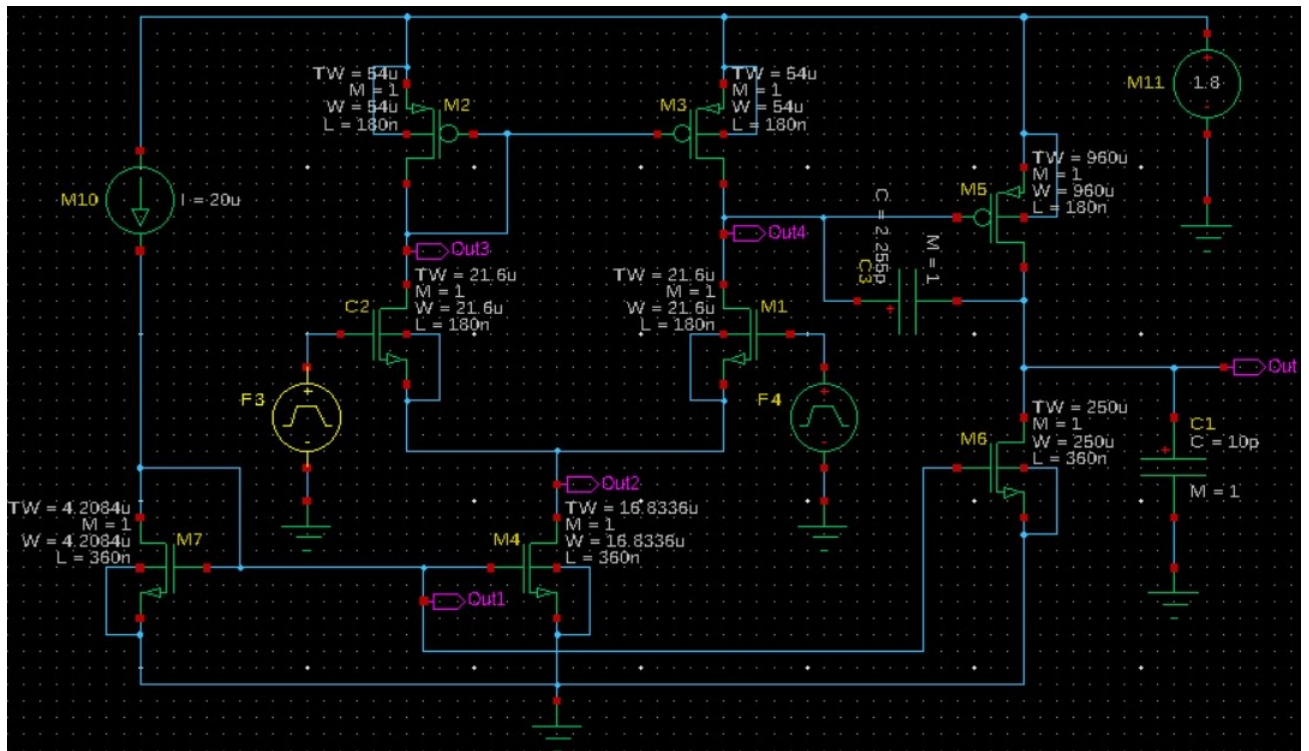


Figure 12: Schematic for Slew Rate

 


Figure 13: Plot for Slew Rate

Table 1: Aspect Ratios of each transistor and capacitances used in the circuit

Transistor	W/L ratio	Capacitor	Value
M1	2160 nm/180 nm	C_C	2.255 pF
M2	2160 nm/180 nm	C_L	10 pF
M3	54000 nm/180 nm		
M4	54000 nm/360 nm		
M5	16833 nm/360 nm		
M6	960 μ m/180 nm		
M7	250 μ m/360 nm		
M8	4.208 μ m/360 nm		

Variable	Theoretical	Practical
Gain	40dB	59.6dB
Gain-Bandwidth	70 MHz	70.00678 MHz
CMRR		-12.28dB
PSRR		-0.066dB
Phase-Margin	60	59.066
Bandwidth		90.867 kHz
ICMR		0.058-1.29V
OCMR		0.028-1.2V
Slew Rate	1 V/ μ s	13.615 V/ μ s

Table 2: Comparison between theoretical and experimental Values obtained

6 CONCLUSIONS

- Designed and implemented 2-stage opamp with high gain bandwidth.
- The assumption that the phase margin is 60 degrees is satisfied.
- Possible minimum lengths taken to achieve high gain bandwidth.
- The Practical value of C_c is taken smaller than the theoretical to achieve high GBW and optimal phase margin as these parameters are inversely proportional to it.
- Results obtained match with theoretical values.